

Use a transistor as a heater

REC Johnson, B Lora Narayana, and Devender Sundi, Center for Cellular and Molecular Biology, Hyderabad, India - April 19, 2012

It is common to use transistors for driving resistive heating elements. However, you can use the heat that a power transistor dissipates to advantage in several situations, eliminating the need for a separate heating element because most transistors can safely operate at temperatures as high as 100°C. A typical example is in a biological laboratory, in which the need for maintaining the temperature of samples in microliter-sized cuvettes is a common requirement. The space/geometry constraint and the less-than-100°C upper-temperature limit are the basic factors of the idea.

You can use an N-channel IRF540 MOSFET to directly heat and control the temperature of a biological sample from ambient to 45°C. **Figure 1** shows a simple on/off-type control circuit in which an LM35, IC₁, is the temperature sensor, whose output a DPM (digital panel meter) can display. IC₂ compares the voltage that VR₁ sets with the output of the LM35 to turn on Q₂ accordingly, with the positive feedback through R₉ providing a small amount of hysteresis. S₁ switches the DPM between a set value and the actual temperature readout. You derive the reference voltage from a TL431 shunt regulator (not shown). The LED lights up when Q₂ is on.

